

GSE/M-21**1498****COMPUTER SCIENCE****(Logical Organization of Computer)****Paper-II**

Time : Three Hours]

[Maximum Marks : 40

Note : Attempt *five* questions in all, selecting *one* question from each unit. Q. No. 1 is compulsory.

Compulsory Question

1. (a) Prove that 2421 is self complimenting.
- (b) State and prove Demorgans' Law.
- (c) Make TT of three variable NOR and AND gate.
- (d) Define Duality principle. 8

UNIT-I

2. Convert as follows :
 - (a) (i) $(7.625)_{10}$ to Binary, Octal and Hexadecimal.
 - (ii) What is number in Binary and Octal for C2BF7 ?
 - (iii) What is $(X)_2 = (2345)_6$?
 - (iv) (101010111110) to Octal and Hexadecimal.
- (b) Write coding scheme for 8421 and for Error Detection and Correction system. 8

3. (a) Write Note on Floating point Notation.
(b) Perform 2's compliment arithmetic.

-22 -12 and -36-17

8

UNIT-II

4. (a) Define Boolean algebra and write its postulates.
(b) Solve Using Boolean Algebra

(i) $(x + y)(xz + z) (\overline{y + xz}) = \overline{xyz}$.

(ii) $ab + bc + ca$.

8

5. (a) Draw and Label 4 Variable K-Map and solve for four corners.

OR

Make Venn Diagram for OR, NAND and XOR gates.

(b) (i) Solve using K-Map $Z = \Sigma 1,3,5,7,9,13,15$

(ii) Solve using K-Map $Z = \pi 0,2,4,6$.

8

UNIT-III

6. (a) Draw T.T and Gates for OR and NAND, NOR and XOR Gates.

8

(b) Make circuit using logic gates for Full Adder.

7. (a) Make circuit and explain 4 : 1 Multiplexer and 10 to 4 line encoder.

8

(b) Make 10 to 4 line Encoder.

UNIT-IV

8. Explain Clocked SRFF, its problem and solution. 8
9. (a) Make Mod-5 Counter using JKFF.
- (b) Make Shift register to store 1011. 8
-